

# The Cutting Edge of Power Electronics for High-Power Applications


---

Hirofumi Akagi

Tokyo Institute of Technology

July 28, 2015



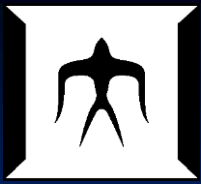

# Tokyo Institute of Technology



**Established in 1881**

# Environmental Energy Innovation (EEI) Building with 650-kW Photovoltaic, 100-kW Fuel-Cell, and 100-kWh Lithium -Ion Battery Energy Storage Systems



# Energy Efficiency of Passenger Aircrafts

## Airbus A340-300

Number of seats: 261

Max. take-off weight: 250,000 kg

Range: 12,800 km

Cruising speed: 875 km/h

**Fuel Consumption (Energy Efficiency):**

**0.039 liters per seat/km**



**A340-300**

## Airbus A330-300

Number of seats: 261

Max. take-off weight: 233,000 kg

Range: 9,700 km

Cruising speed: 875 km/h

**Fuel Consumption (Energy Efficiency):**

**0.035 liters per seat/km**

**A330-300**



source: SCANORANAM, FEB 2007



# What is Power Electronics? (1/2)

- **The IEEE Power Electronics Society** with a membership of 8,000 is one of some 40 IEEE Societies.
- **Power Electronics** is based on **switching operation** of power semiconductor devices such as **MOSFETs** and **IGBTs** for achieving efficient power conversion.
- **Power Electronics Technology** encompasses
  1. the effective use of electronic components,
  2. **the application of circuit and control theory**,
  3. the development of analytical tools toward conversion, **control**, and conditioning of electric power.



# What is Power Electronics? (2/2)

- Power range: from **several watts** to **6.3 GW**
- Frequency range: from **0 Hz (dc)** to **13.56 MHz**
- Devices: semiconductors, magnetics, and capacitors
- **Controls**: DSPs, PLDs, FPGAs, A/D converters, and sensors of voltage, current, magnetic flux, position, speed, acceleration, temperature, etc.

**Power Electronics** is on the basis of  
**Devices, Circuits, Controls, and Systems**



# Practical Applications of Power Electronics

- Switching power supplies for computers and servers
- Home appliances: **air conditioners**, refrigerators, induction-heating cookers, microwaves, vacuum cleaners, laundry machines, electric fans, LED lamps, and so on.
- UPS (uninterruptable power supply): from 1 kW to 1 MW
- Industrial induction heating: **200 kHz 200 kW for surface quenching**
- Industrial ac motor drives: fans/blowers, pumps, compressors, steel mills, and so on
- Transportation: high-speed and commuter trains, trams/street cars, electric vehicles, fuel-cell vehicles, ships/boats, and aircrafts
- Electric power utilities: **photovoltaic inverters, battery energy storage systems**, adjustable-speed pumped hydro storage, reactive-power controllers, **high-voltage dc transmission systems**



# **A Flexible, Effective, and Fault-Tolerant Battery Energy Storage System (BESS)**

---


To be published in the IEEE Transactions on Power  
Electronics, or Early access




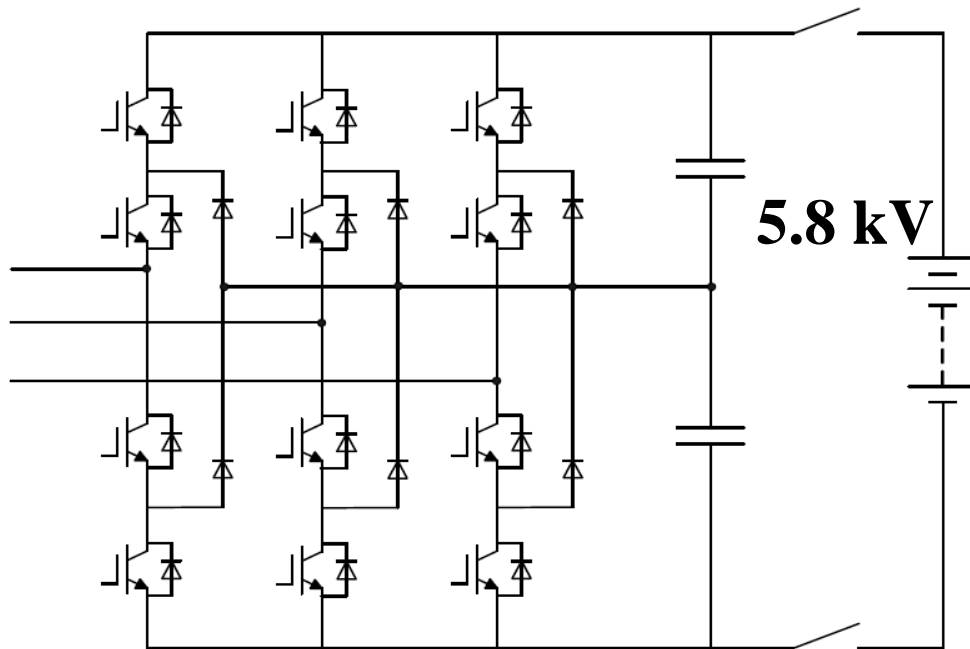
# An Existing Battery Energy Storage System (BESS)

N. Wade, P. Taylor, P. Lang, and **J. Svensson**, “Energy storage for power flow management and voltage control on an 11kV UK distribution network,” in *Proc. CIRED’09*, Jun. 2009.




- EDF Energy Networks, UK
- **600-kW 200-kWh BESS for peak shaving**
- **Neutral-Point Clamped (NPC) Converter[1]**
- **Li-ion battery system**

[1] A. Nabae, I. Takahashi, and H. Akagi, “A New Neutral-Point-Clamped PWM Inverter,” *IEEE Trans. Industry Applications*, vol. 17, no. 5, pp. 518-523, Sep./Oct. 1981. **Cited by 3214**


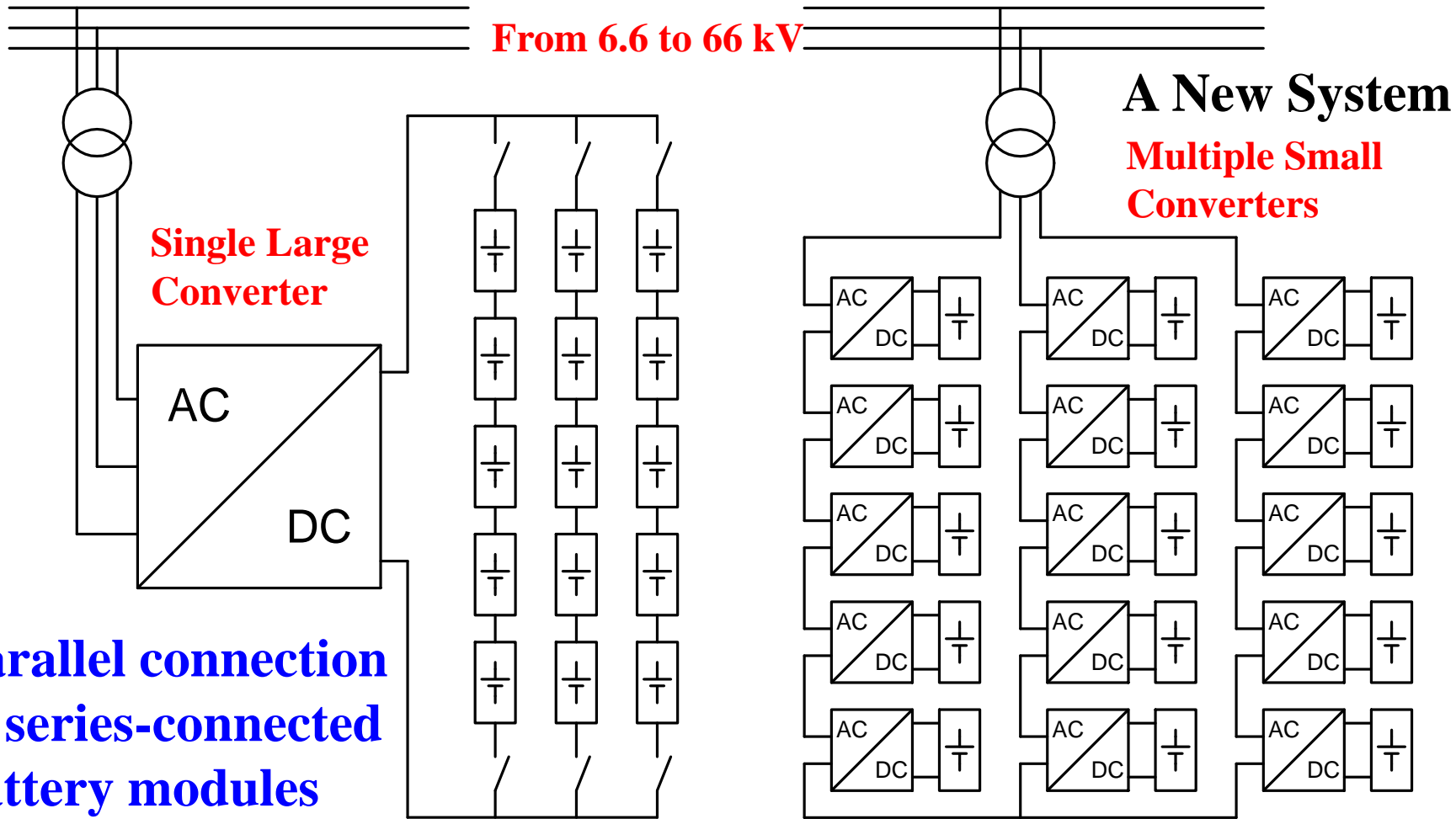
# Comparisons between Existing and New BESSs



**Single Large Converter**


**A New System**  
**Multiple Small Converters**

**Parallel connection of series-connected battery modules**

**One converter-to-one battery module**

**Existing System**
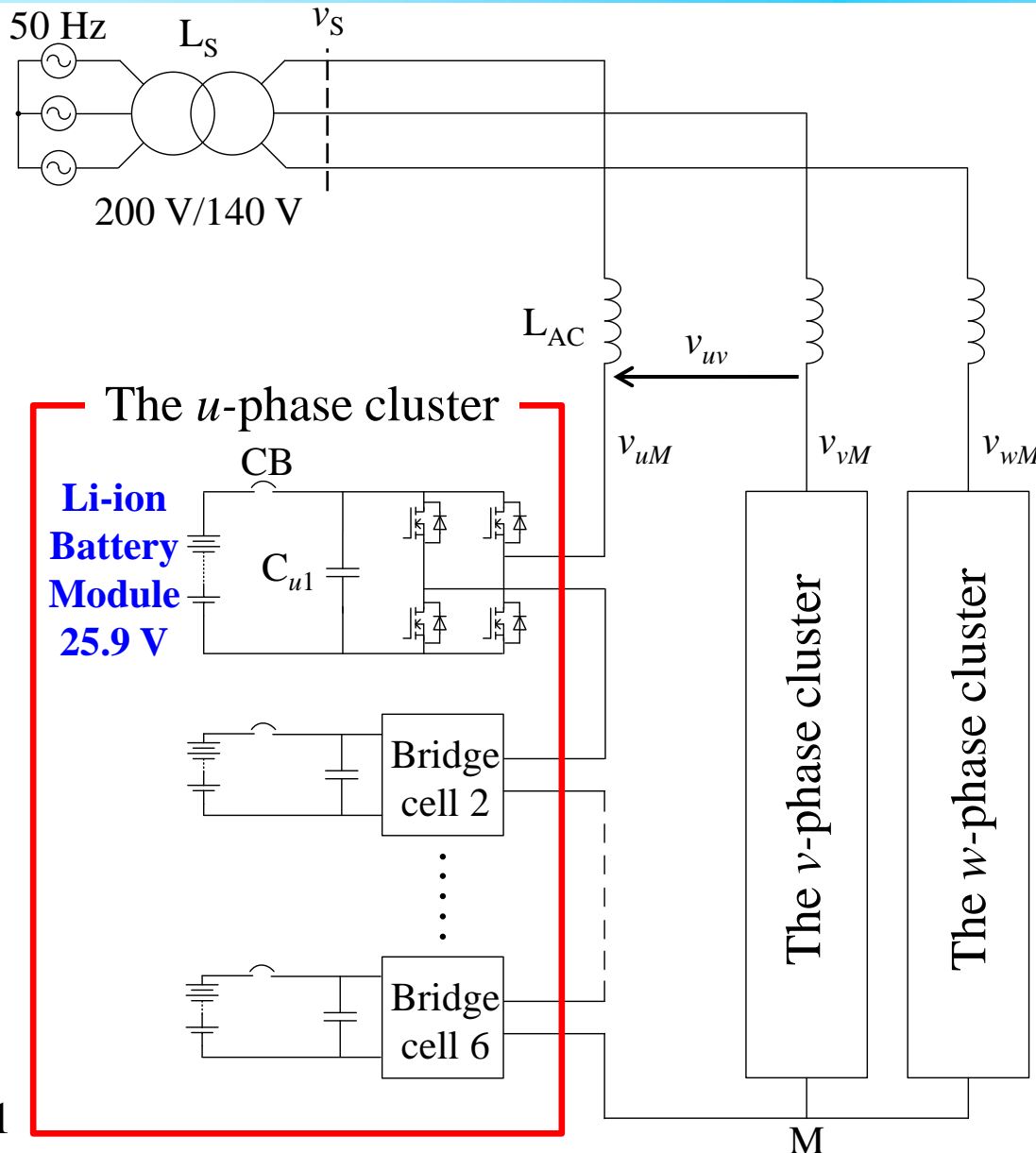
# Three-phase 10-kW, 22-kWh Downscaled System



## Circuit parameters

Nominal line-to-line rms voltage $V_s$	140 V
Rated power	10 kW
Cascade number	6
Background system Inductance $L_S$	0.10 mH (1.6%)
AC link Inductance $L_{ac}$	0.33 mH (5.3%)
DC capacitor capacitance	47 mF
Nominal battery voltage	<b>25.9 V</b>
Each battery capacity	1.2 kWh
PWM carrier frequency $f_c$	<b>1.75kHz</b>
Equivalent PWM carrier frequency	<b>21 kHz</b>

# 18 Li-Ion Battery Modules (25.9 V, 47.5 Ah )




Nominal voltage: 25.9 V (=3.7 V/cell times 7 cells)

Weight: 15 kg/module, Total capacity: **22 kWh** *Tokyo Institute of Technology*  
*Power Electronics Lab.*



# Control System

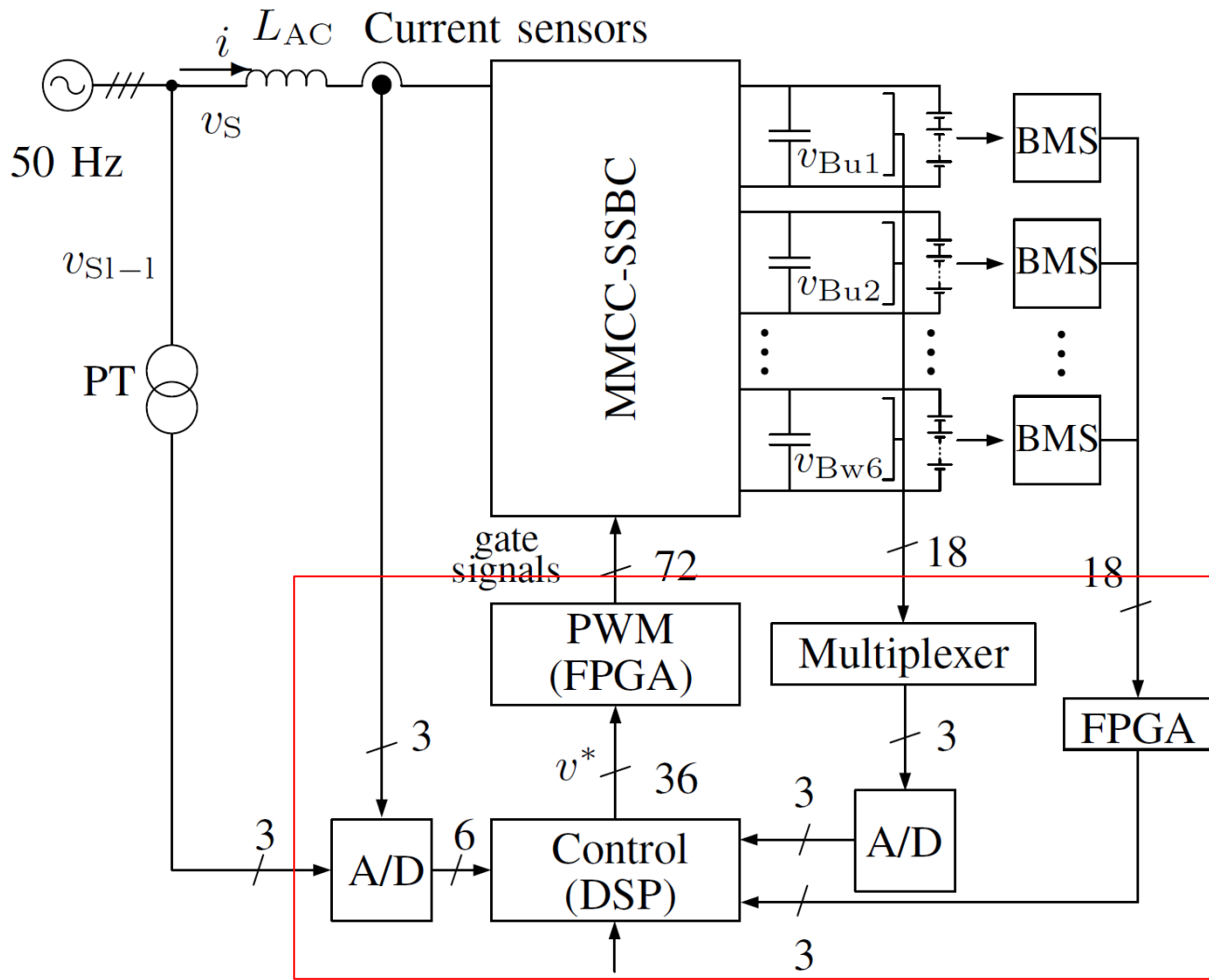

**BMS:**

Battery  
Management  
System

**Signals**


Input: 43

Output: 72

**Digital controller**  $p^*$  (Active-power reference)


# Phase-Shifted-Carrier PWM (One-Cell Update)
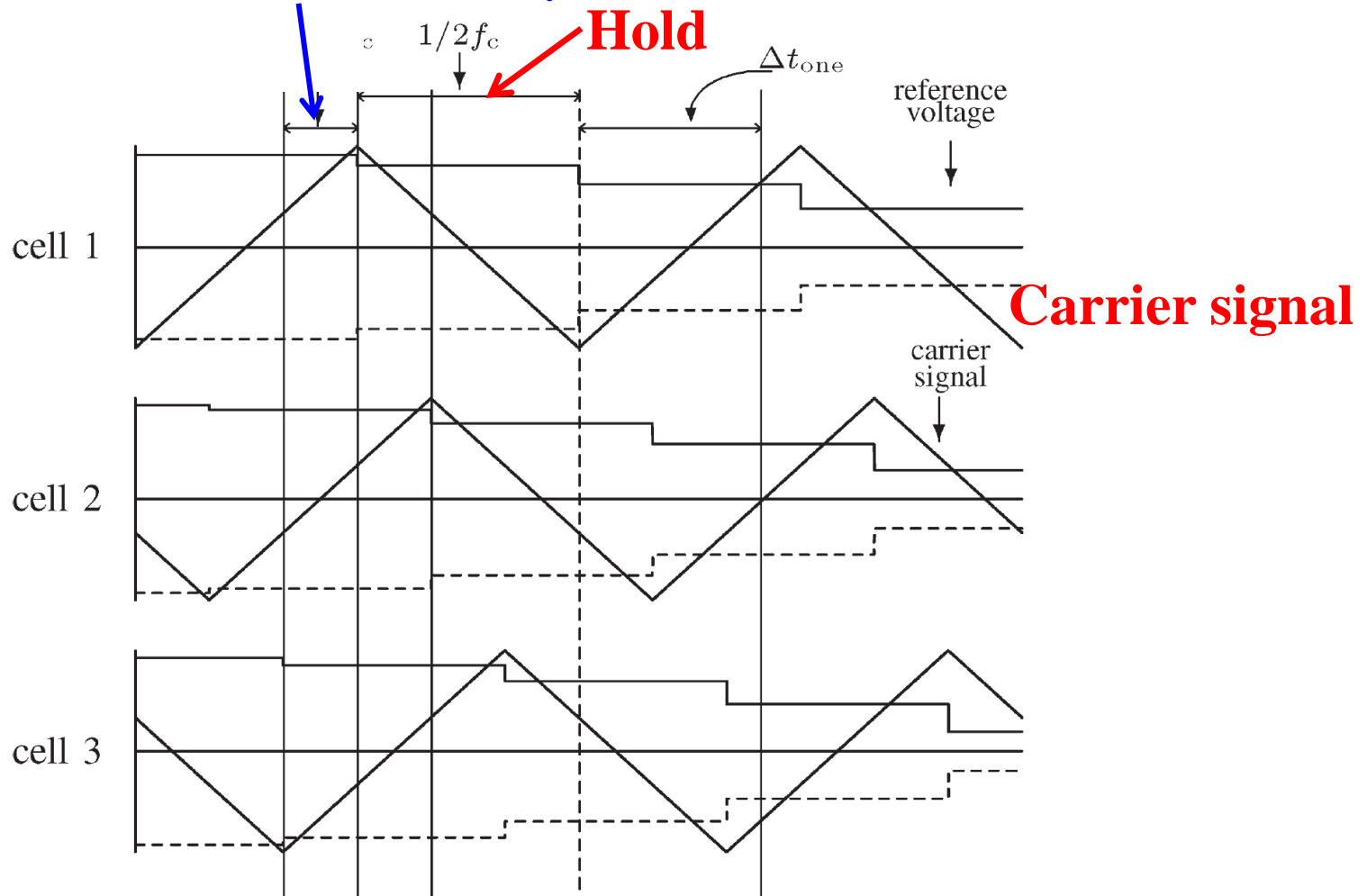
## Calculation (within $40 \mu\text{s}$ )




**Hold time =  $N \times$  Calculation time**
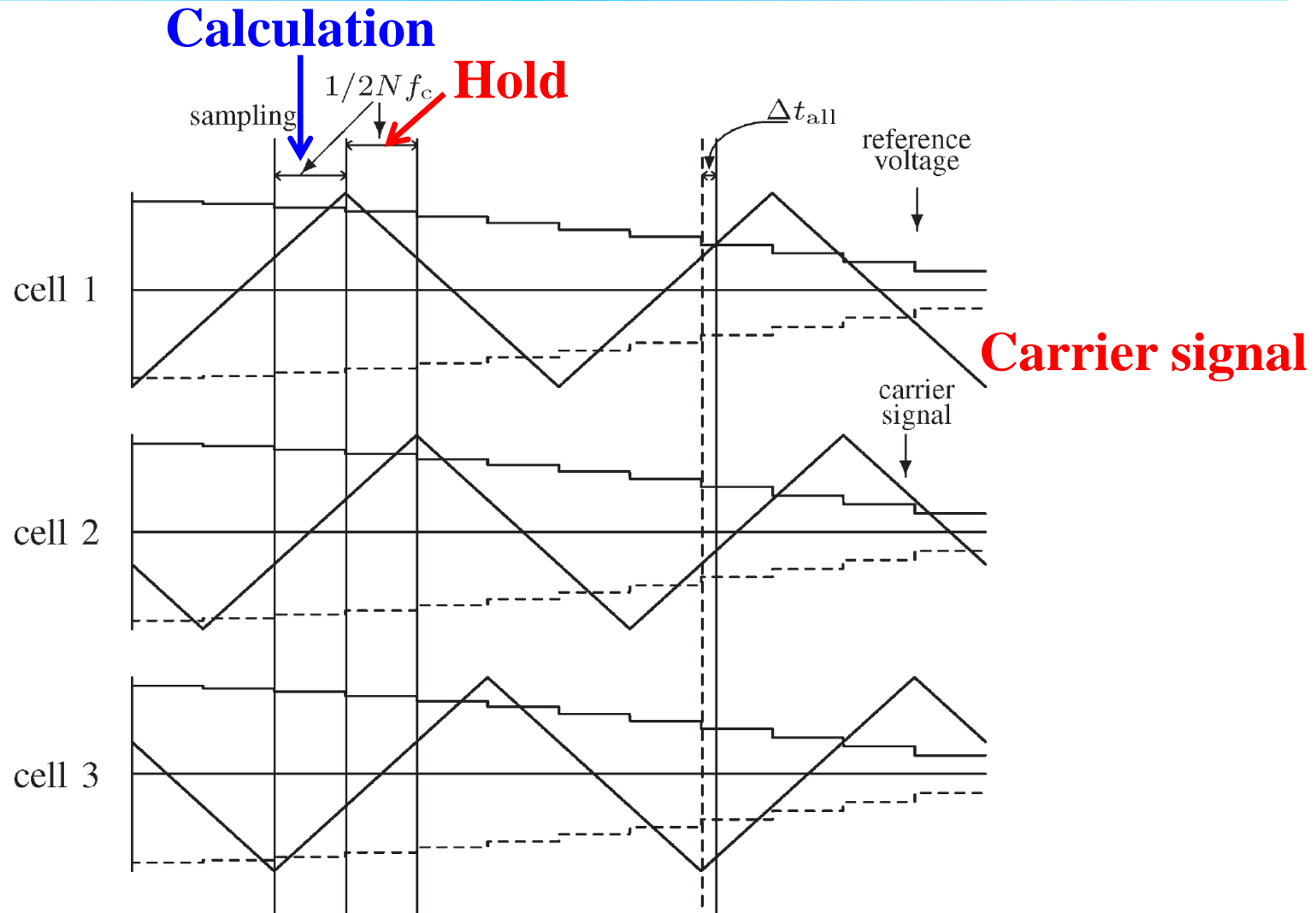
# Phase-Shifted-Carrier PWM (All-Cell Update)



**Hold time = Calculation time**

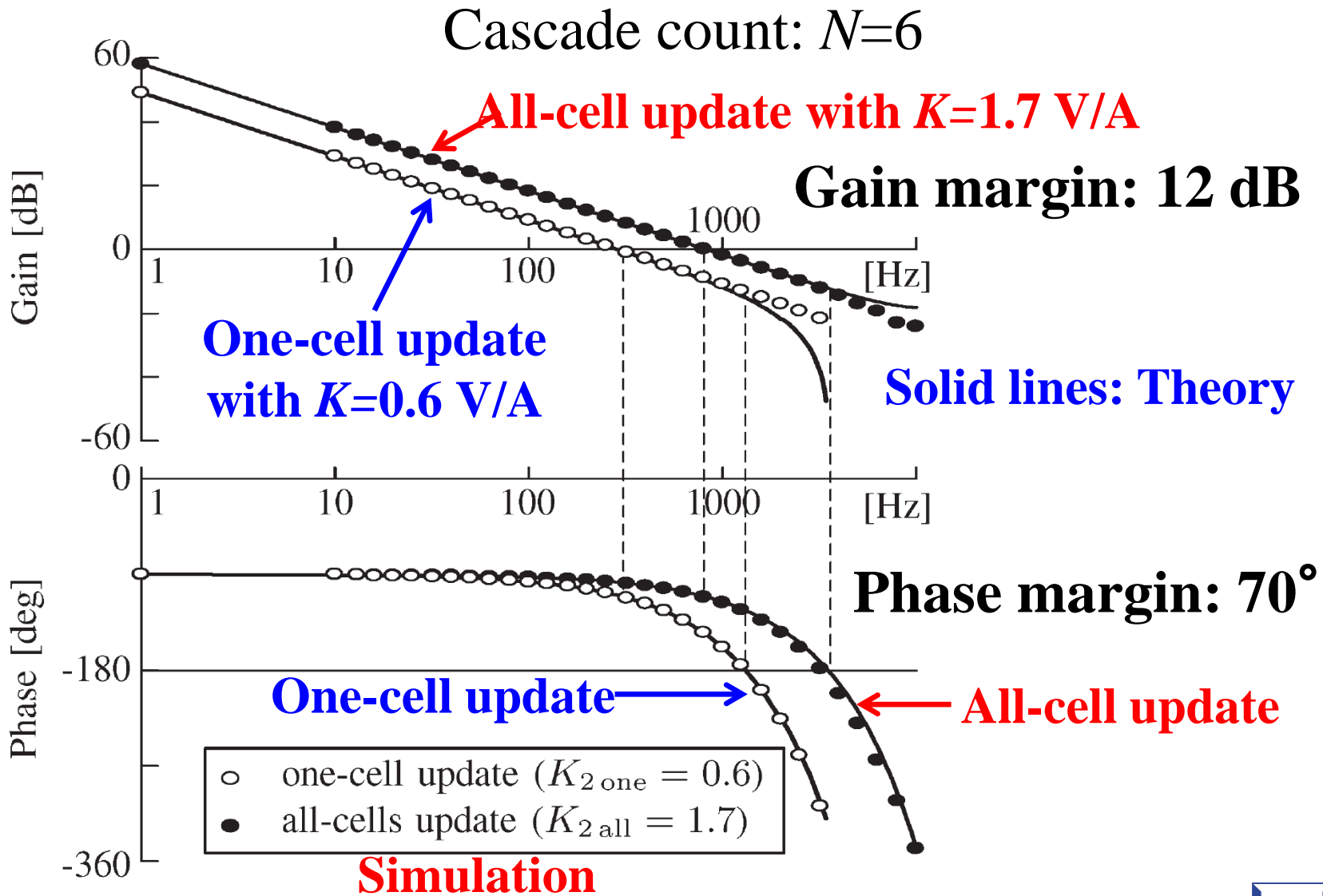
# Comparisons between Theory and Simulation in Open-Loop Transfer Function of Current Control






# Critical Damping Gain vs Cascade Count $N$

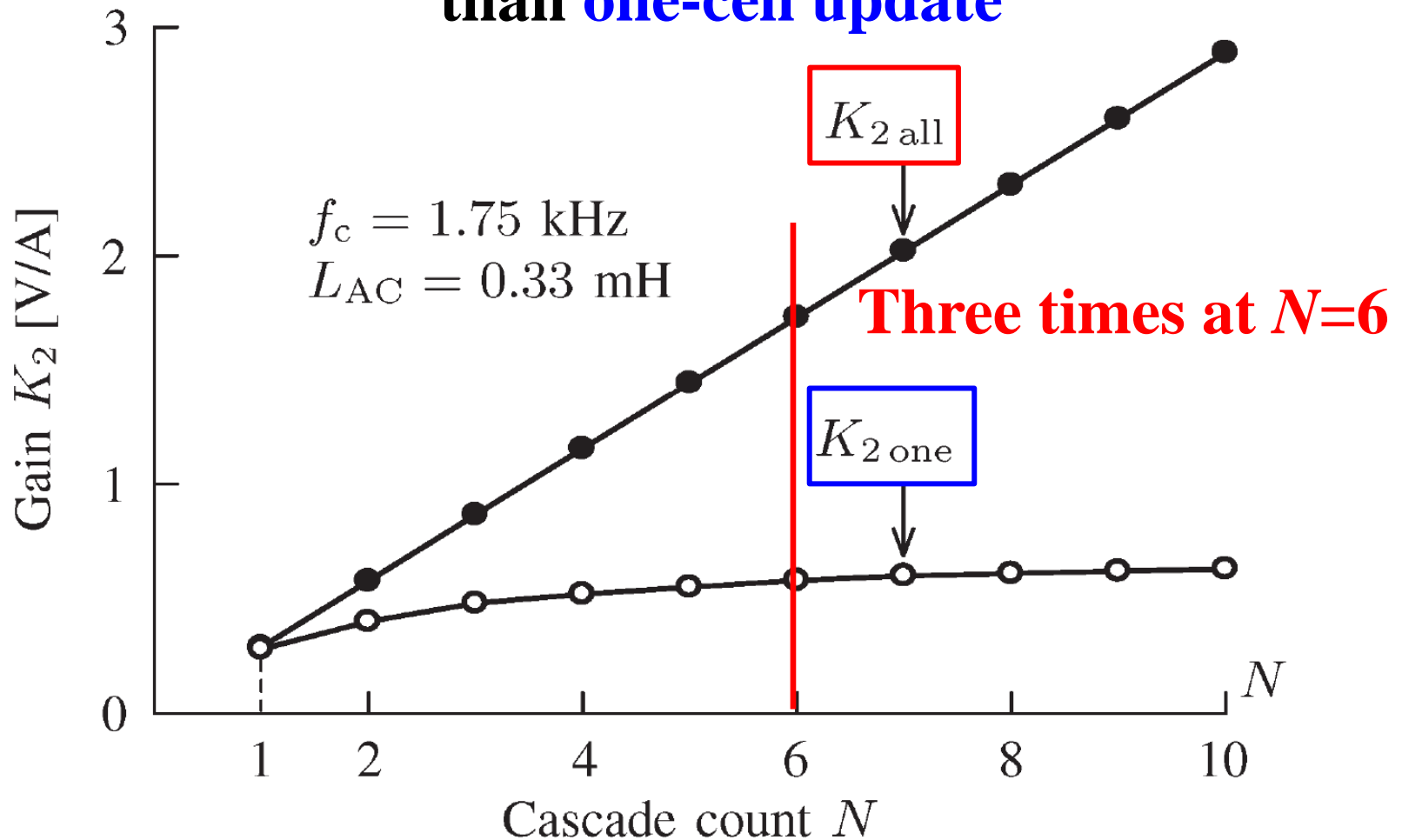**All-cell update** is better in current controllability than **one-cell update**




# Experimental Waveforms (All-cell update)

## Charge mode

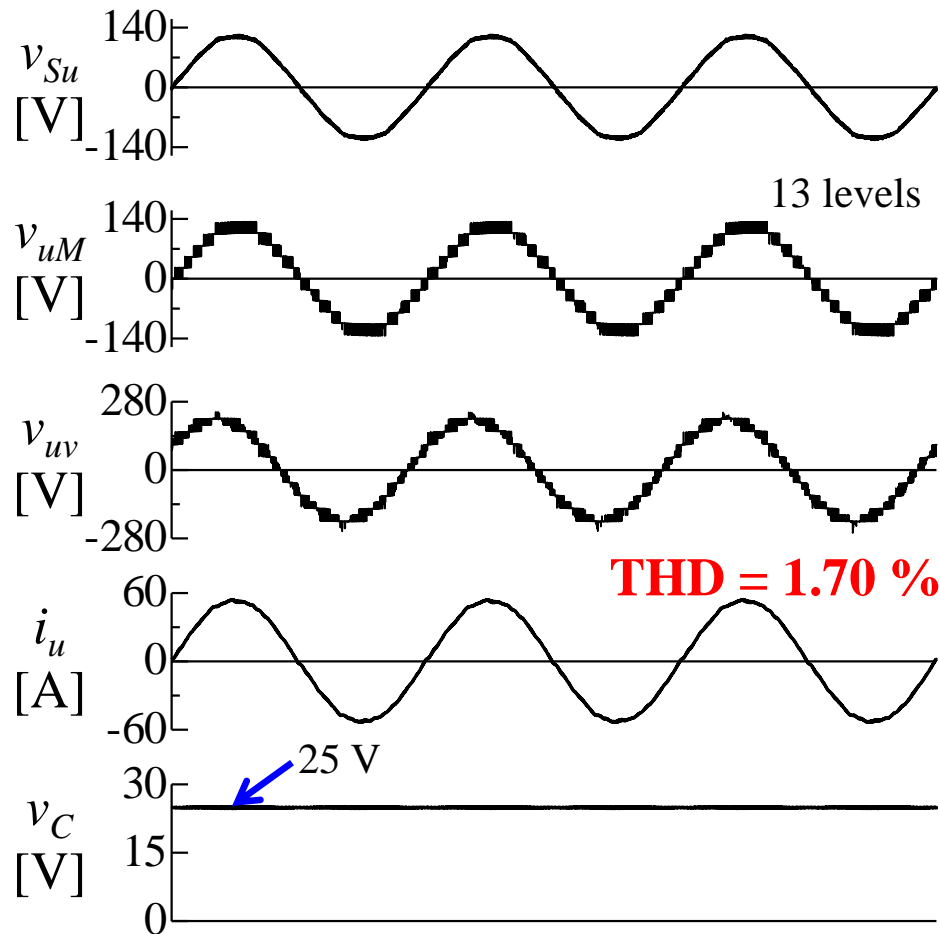

## Discharge mode

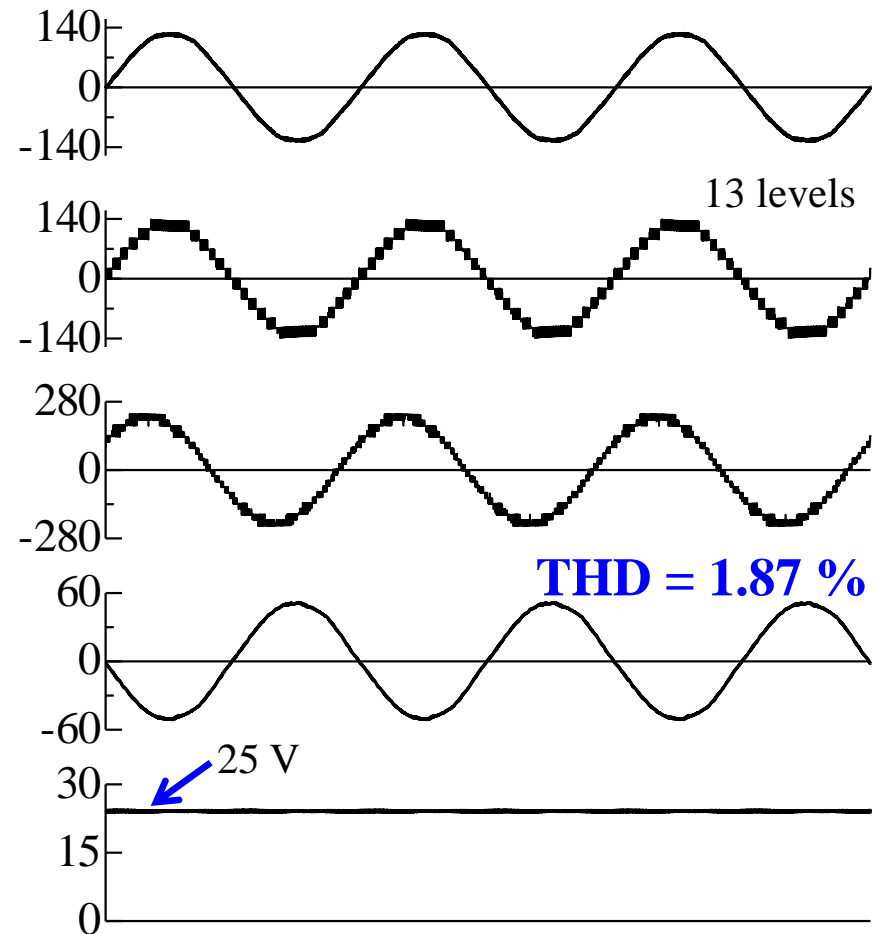


# A Grid-Level High-Power DSCC-Based BTB (Back-To-Back) System Without Common DC-Link Capacitor

---


Published in the IEEE Transactions on Industry Applications,  
vol. 50, no. 4, pp. 2648-2659, July/Aug. 2014



# A Grid-Level DSCC-Based BTB System

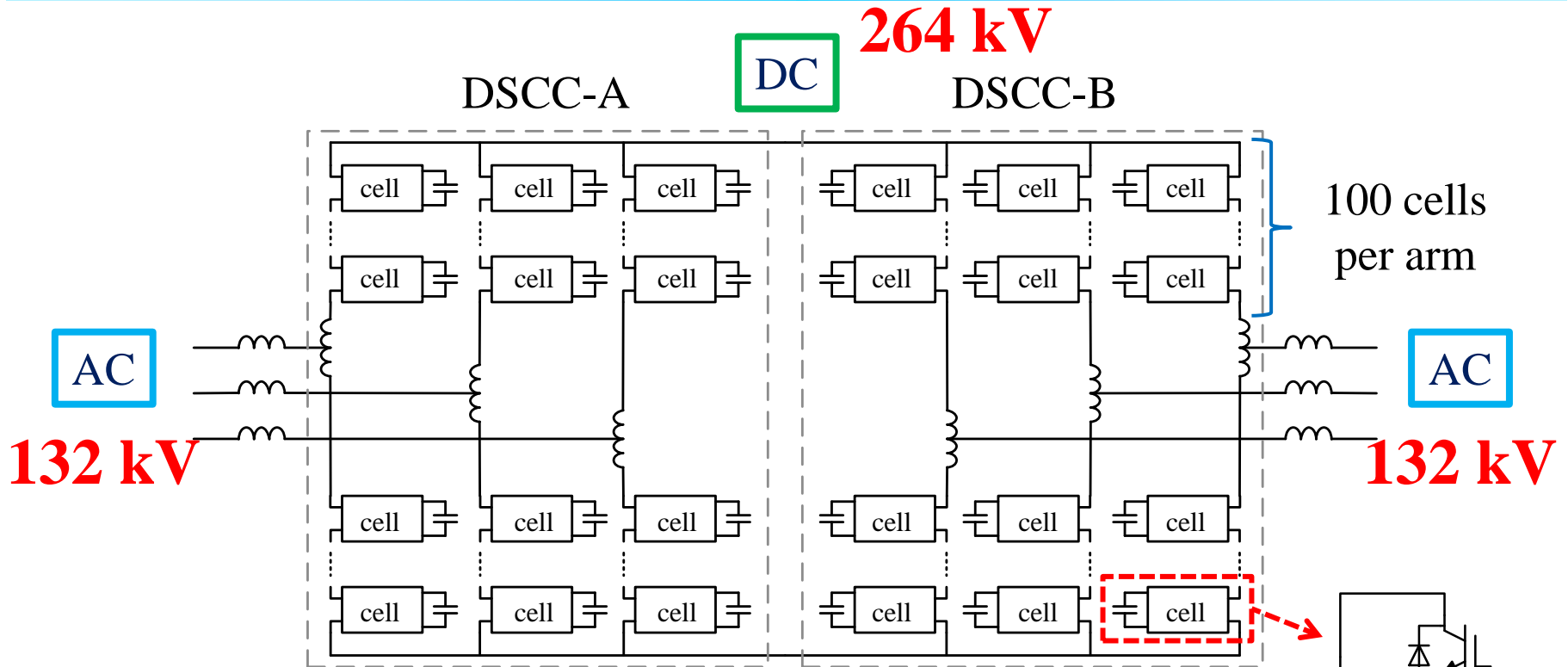

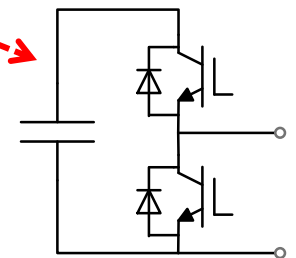
- Self-commuted devices (e.g., high-voltage GCTs)
  - ➔ Fast response, Easy to self-start
- No dc capacitor or voltage sensor at 264-kV dc-link



Bidirectional chopper-cell

# Downscaled BTB Unit for Experiment

Three-phase 200-V, 10-kW BTB system

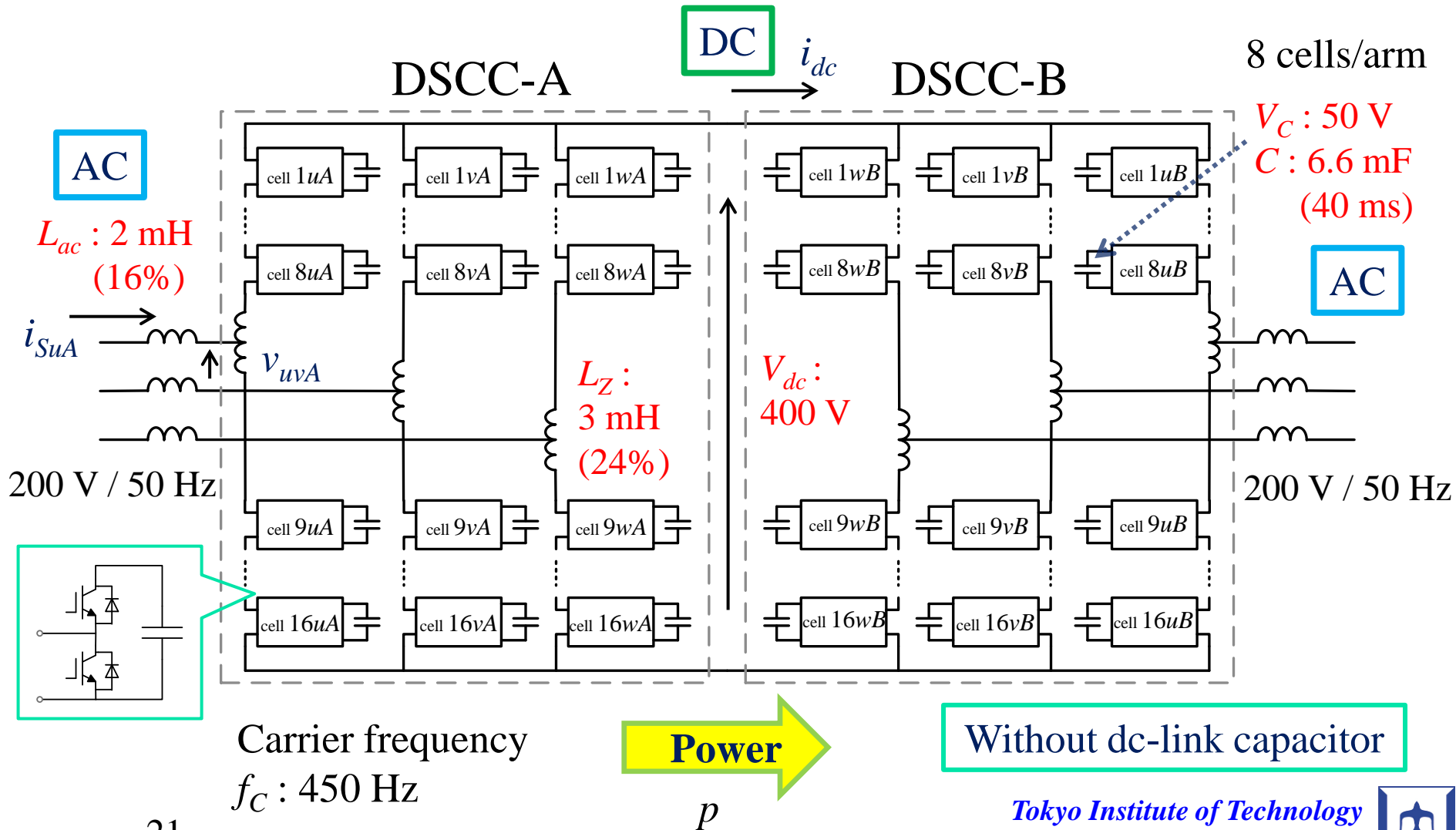

# Photo of three-phase 200-V 10-kW 50-Hz BTB System

DSCC-A

DSCC-B

u-phase

v-phase

w-phase

Module Structure:

16 cells/leg

Chopper Cell:

150-V 70-A

MOSFET  $\times 4 \times 2$

50-V 6.6-mF

Capacitor

Digital Controller:


A DSP board and

Two FPGA boards

PC based data acquisition systems



# Digital Control System

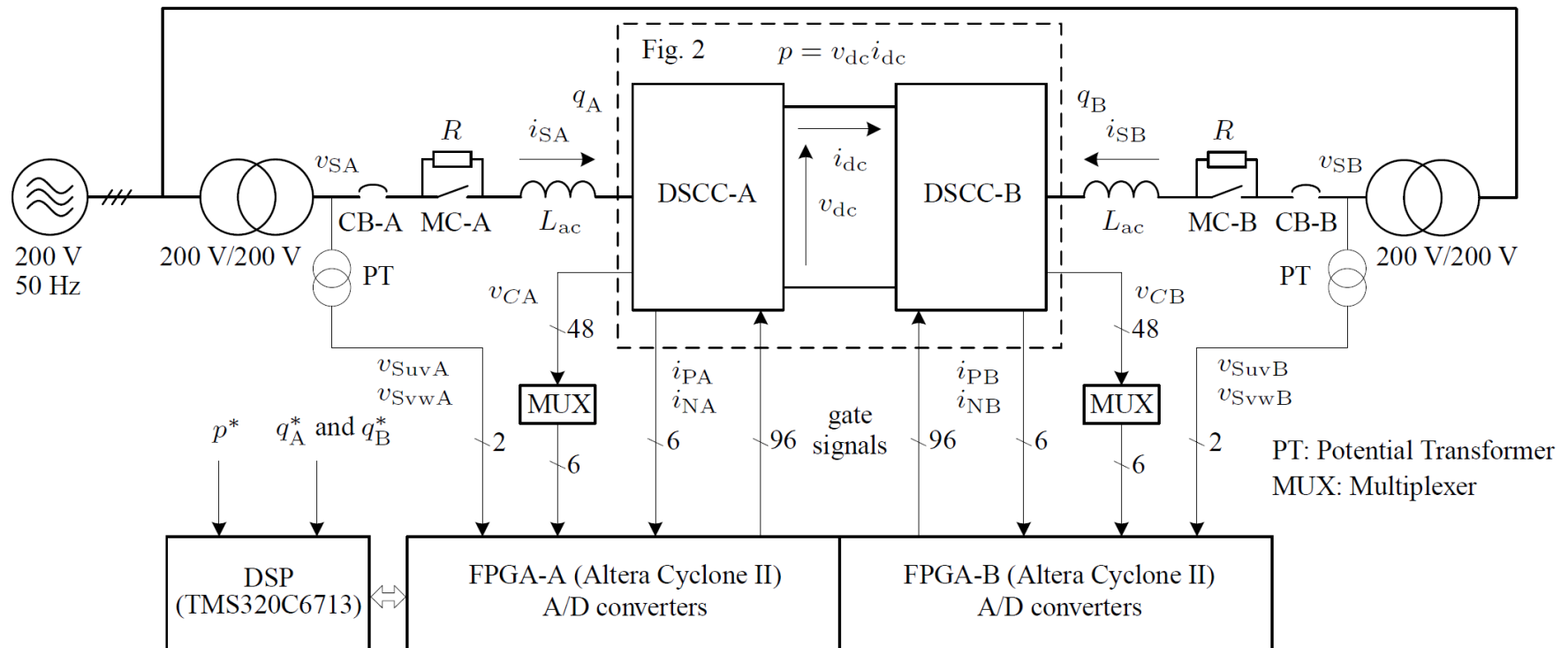

**Detected signals**

Line-to-line voltages	$2 \times 2$
Arm currents	$6 \times 2$
Capacitor voltages	$48 \times 2$

**Output: 192 (= 96 × 2) gate signals**


**Sampling frequencies in digital control**  
 arm currents: 7.2 kHz (= 450Hz × 16)  
 capacitor voltages: 450 Hz



# Rectification (DSCC-A) at $p^* = +8.7 \text{ kW}$ , $q_A^* = -5.0 \text{ kVA}$

## Experiment

## Simulation

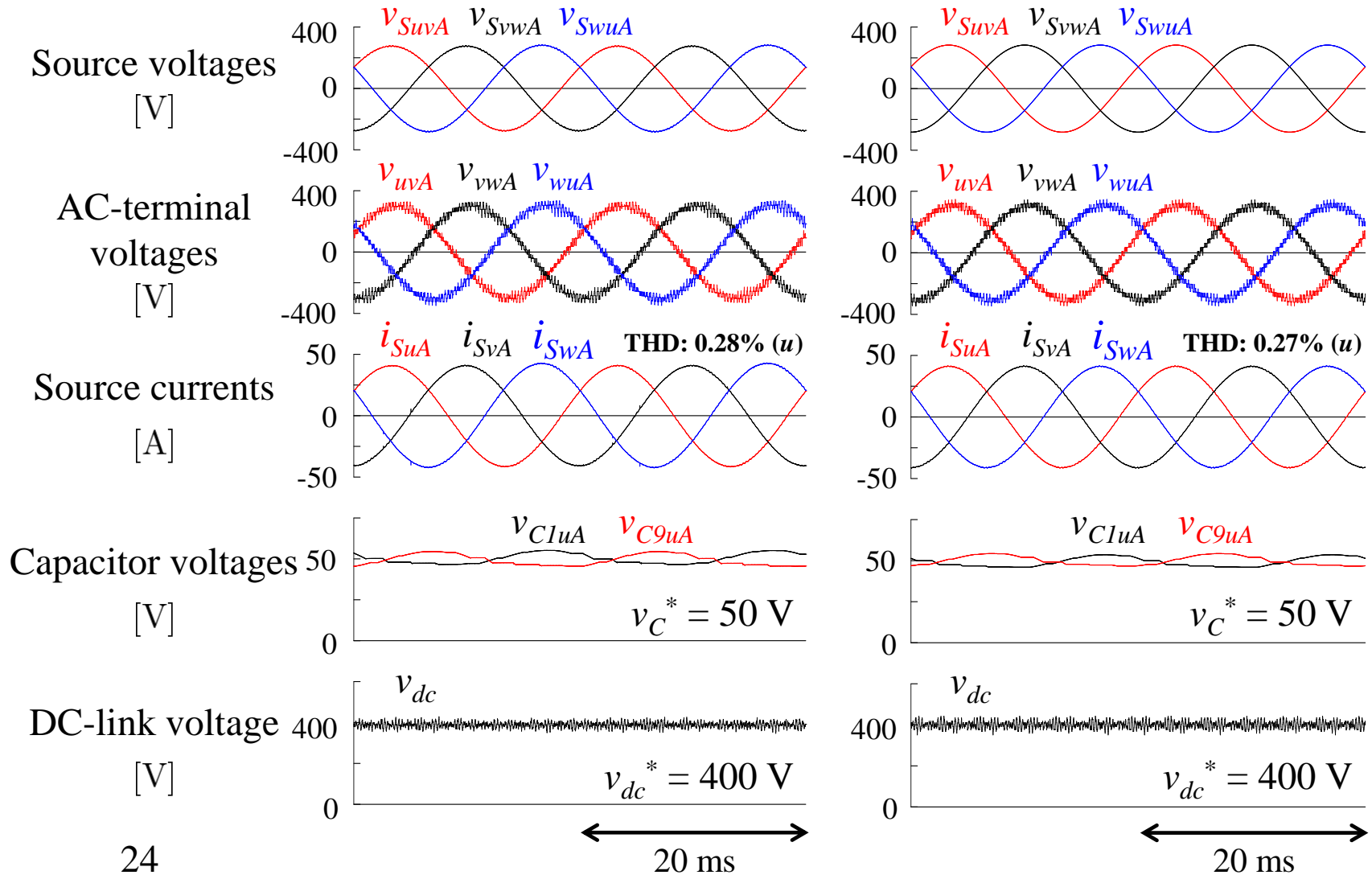




# Transition (DSCC-A) at $p^* = +10 \text{ kW} \rightarrow -10 \text{ kW}$

$$q_A^* = q_B^* = 0$$

**Experiment**

**Simulation**

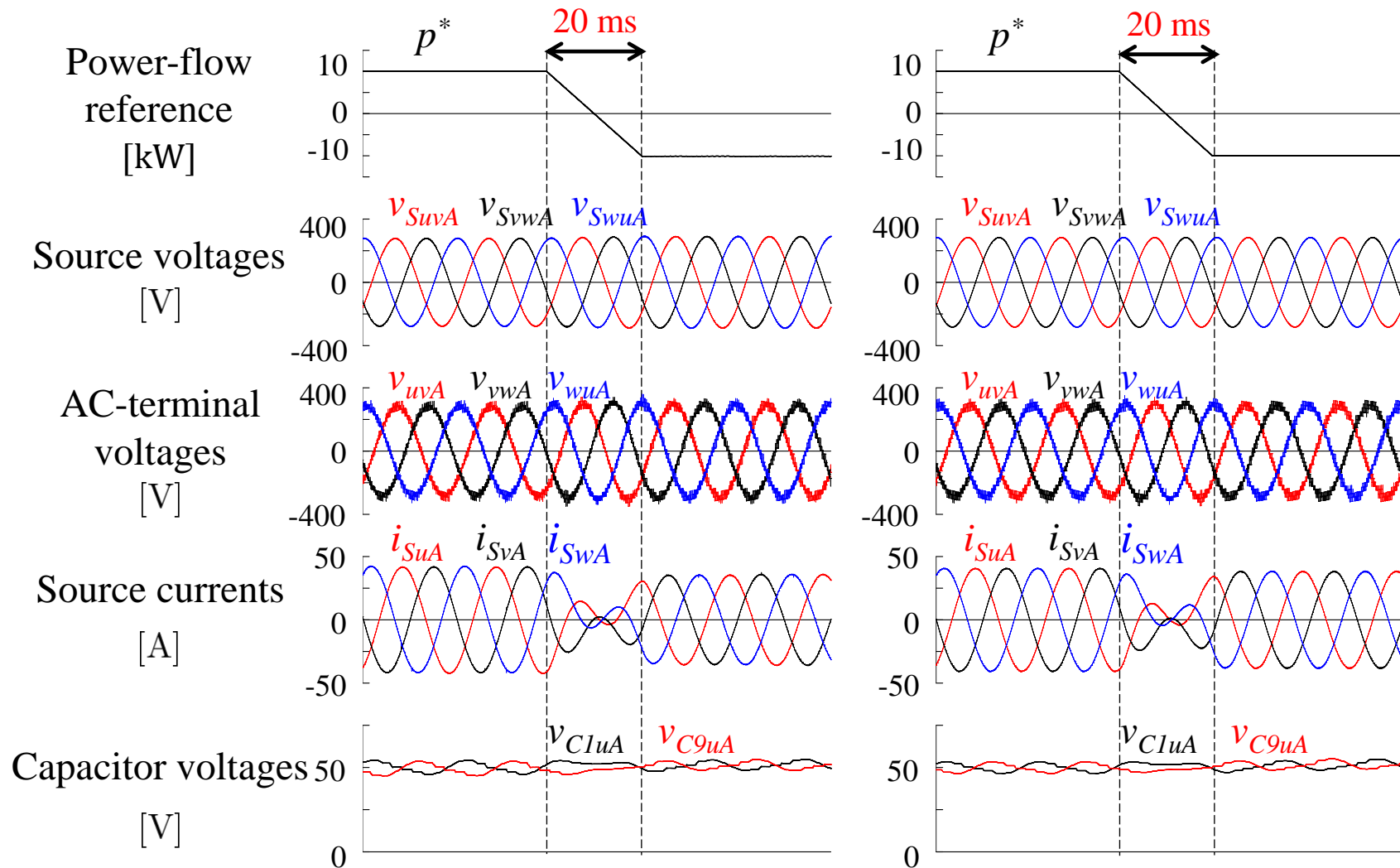

# A Low-Speed, High-Torque Motor Drive Using the Modular Multilevel Cascade Converter Based on Triple-Star Bridge Cells (MMCC-TSBC)

---

To be Published in the 2015 Sep./Oct. Issue of the IEEE Transactions on Industry Applications, or Early access



# Medium-Voltage High-Power Motor Drives



Blower fan from  
Mitsubishi Heavy Industry



Cement mill drive  
from ABB


Line-commutated cycloconverters using thyristors

Problems: Low lagging power factor


Complicated line harmonic currents




# Three-phase 400-V 15-kW TSBC Converter

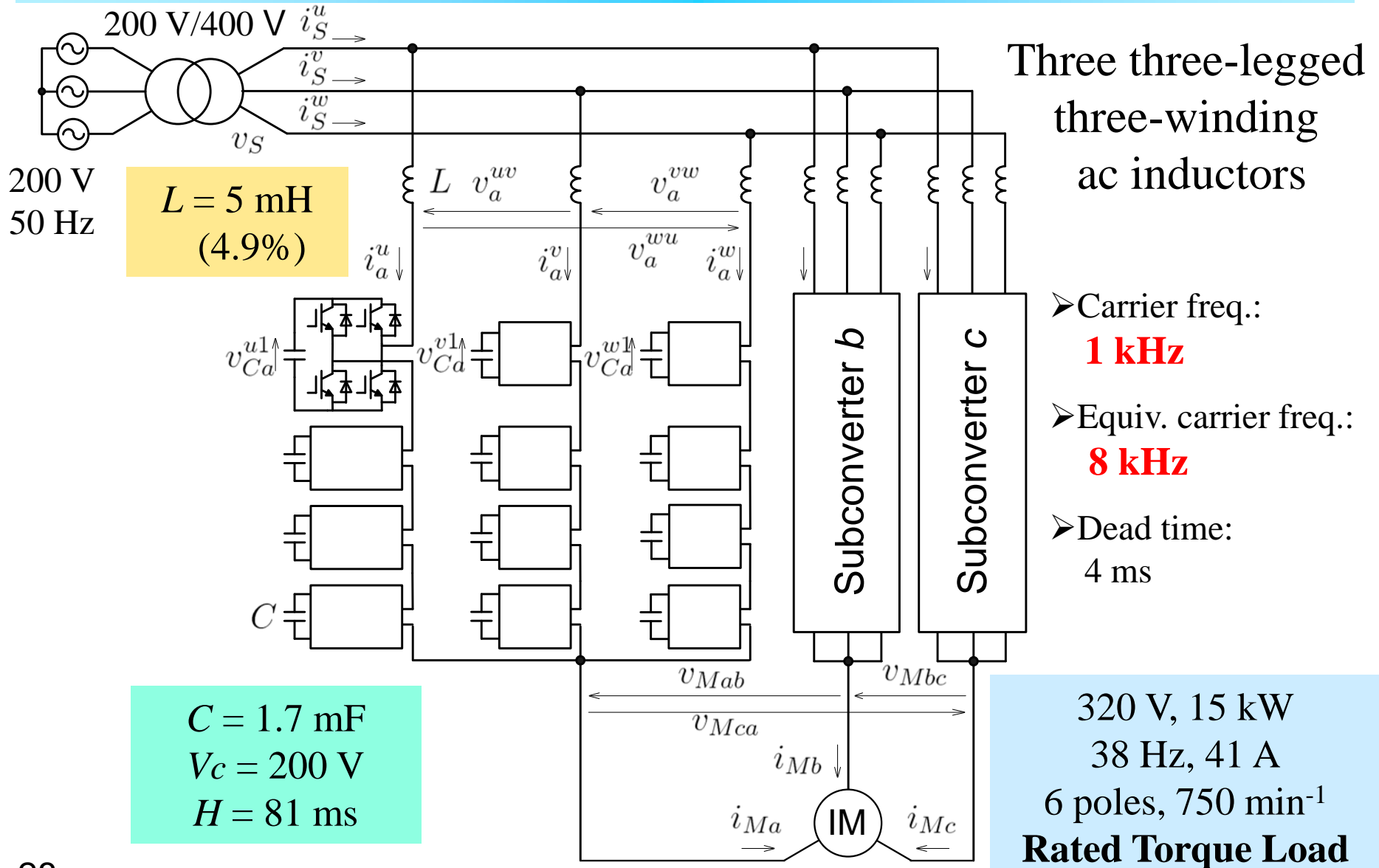

# Overview of the Experimental System

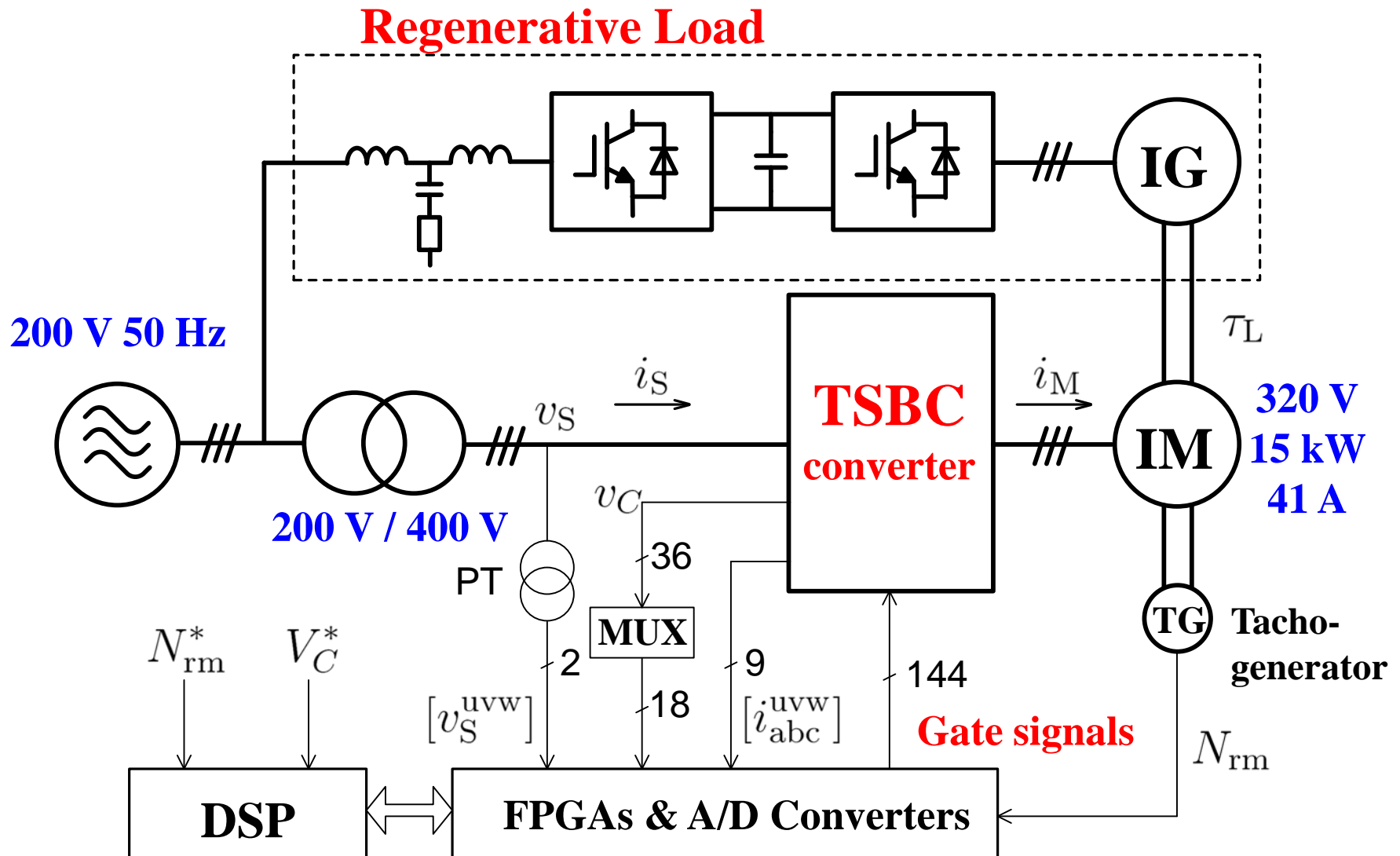
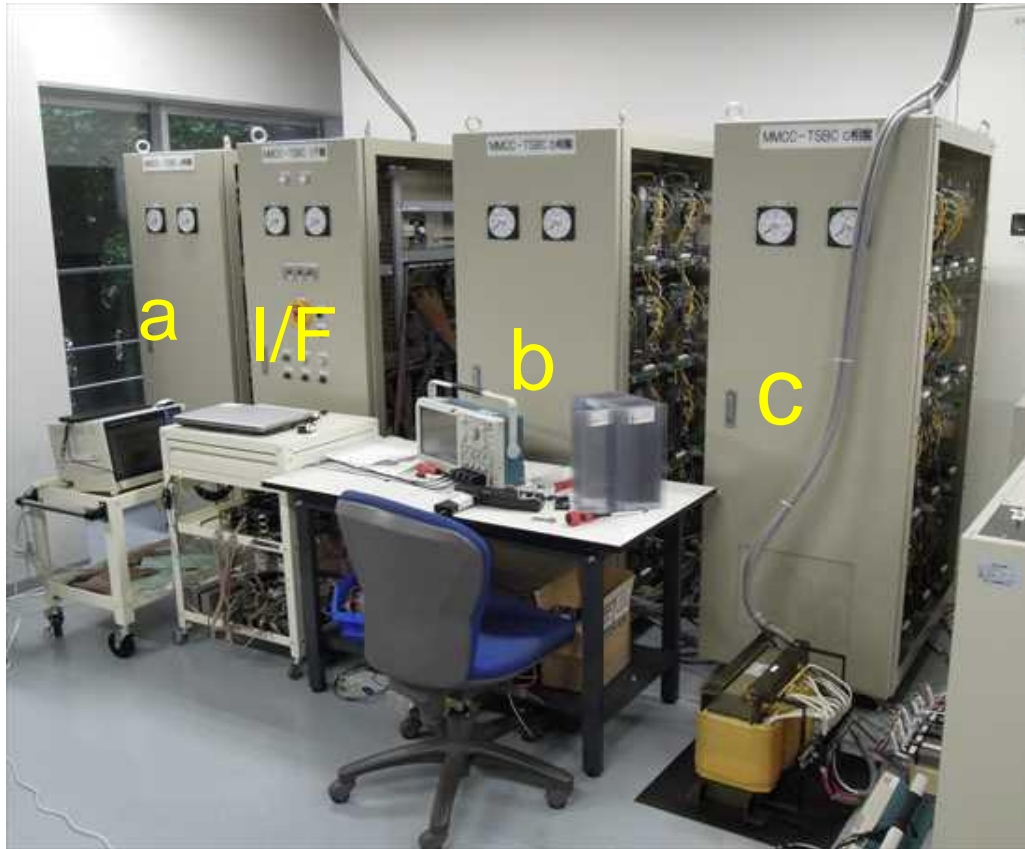
# Three-phase 400-V 15-kW Experimental System



## 4 Bridge Cells per Cluster

- 36 Bridge Cells
- 144 IGBTs

$$L = 5.0 \text{ mH (5\%)}$$

**Three three-legged  
three-winding ac inductors**

$$C = 1.7 \text{ mF}$$


$$V_c = 210 \text{ V (rated)}$$

$$H = 89 \text{ ms}$$

**Carrier frequency: 1 kHz**


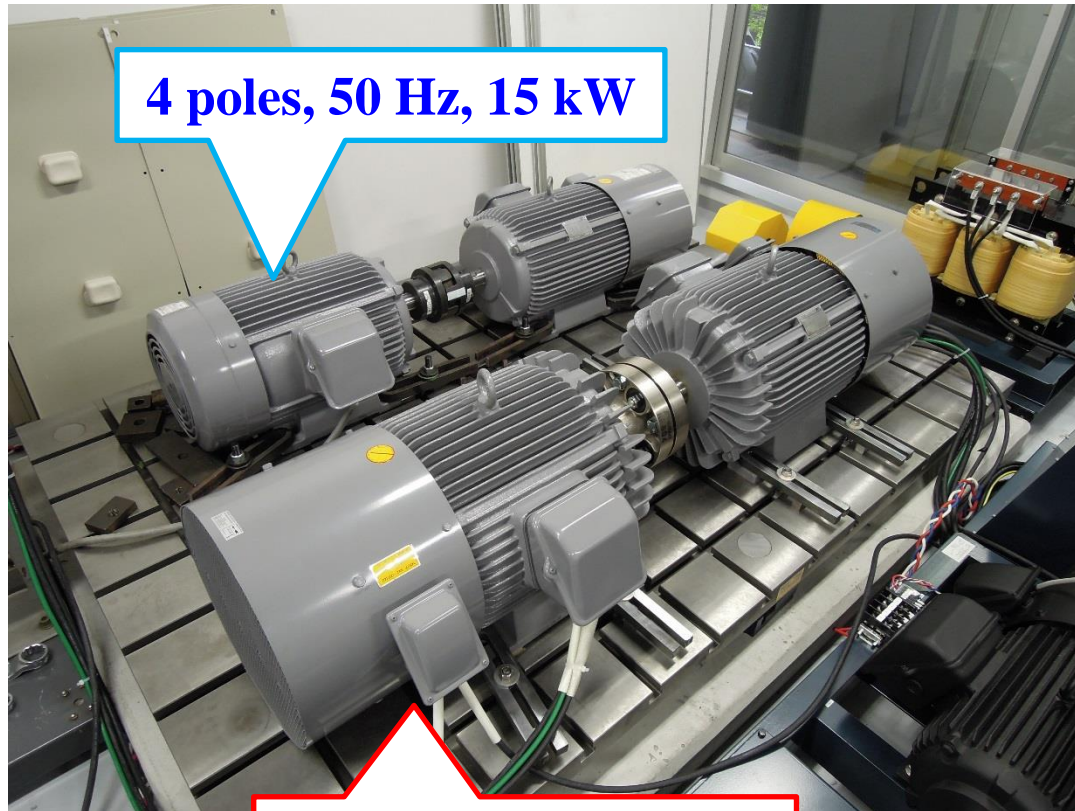
# Three-phase 320-V 15-kW Induction Motor




**6 poles, 38 Hz, 15 kW**

**4 poles, 50 Hz, 15 kW**

	Rated Values
Power	15 kW
Voltage	320 V
Current	41 A
<b>Frequency</b>	<b>38 Hz</b>
Rotating speed	750 r/m
<b>Poles</b>	<b>6</b>
Torque	191 N·m



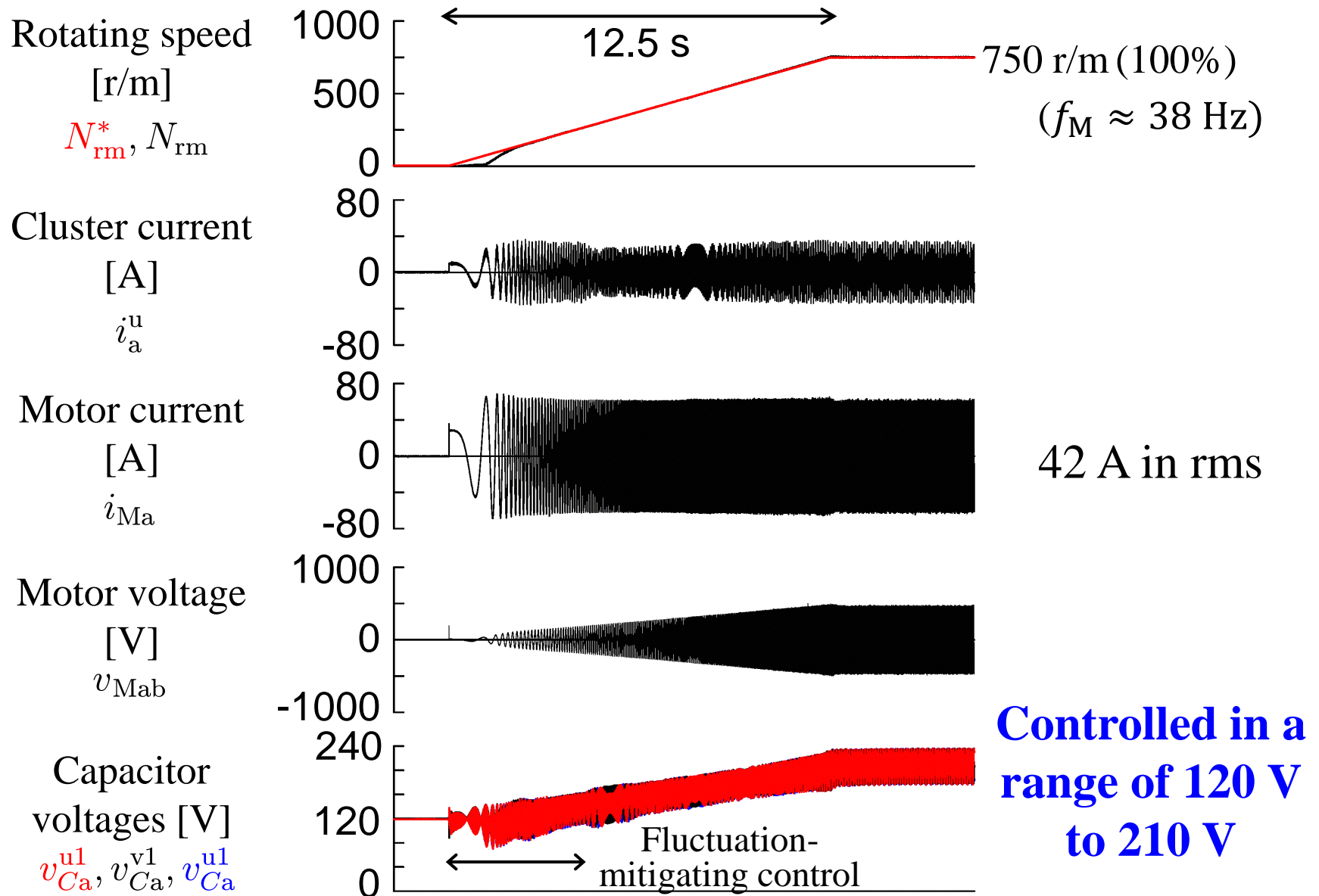
# Start-up Performance Loaded at 100% Torque




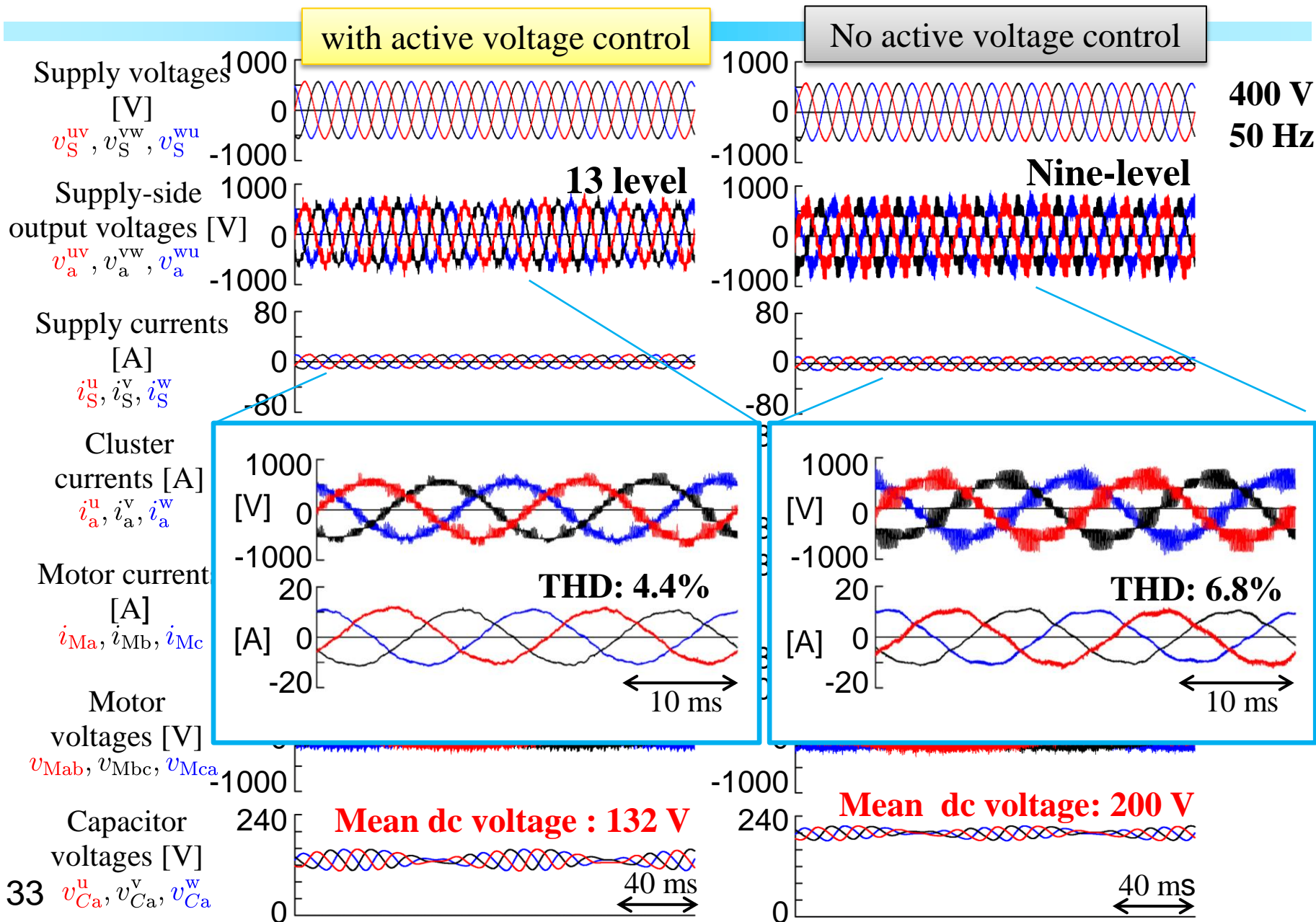
# $N_{rm} = 100 \text{ r/m (13\%)} \text{ Loaded at 100\% Torque}$




# Power-Loss Breakdown of a 750-Vdc, 100-kW, 20-kHz Bidirectional Isolated DC-DC Converter Using SiC-MOSFET/SBD Dual Modules

---

Published in the IEEE Transactions on Industry Applications,  
vol. 51, pp. 420-428, Jan./Feb. 2015


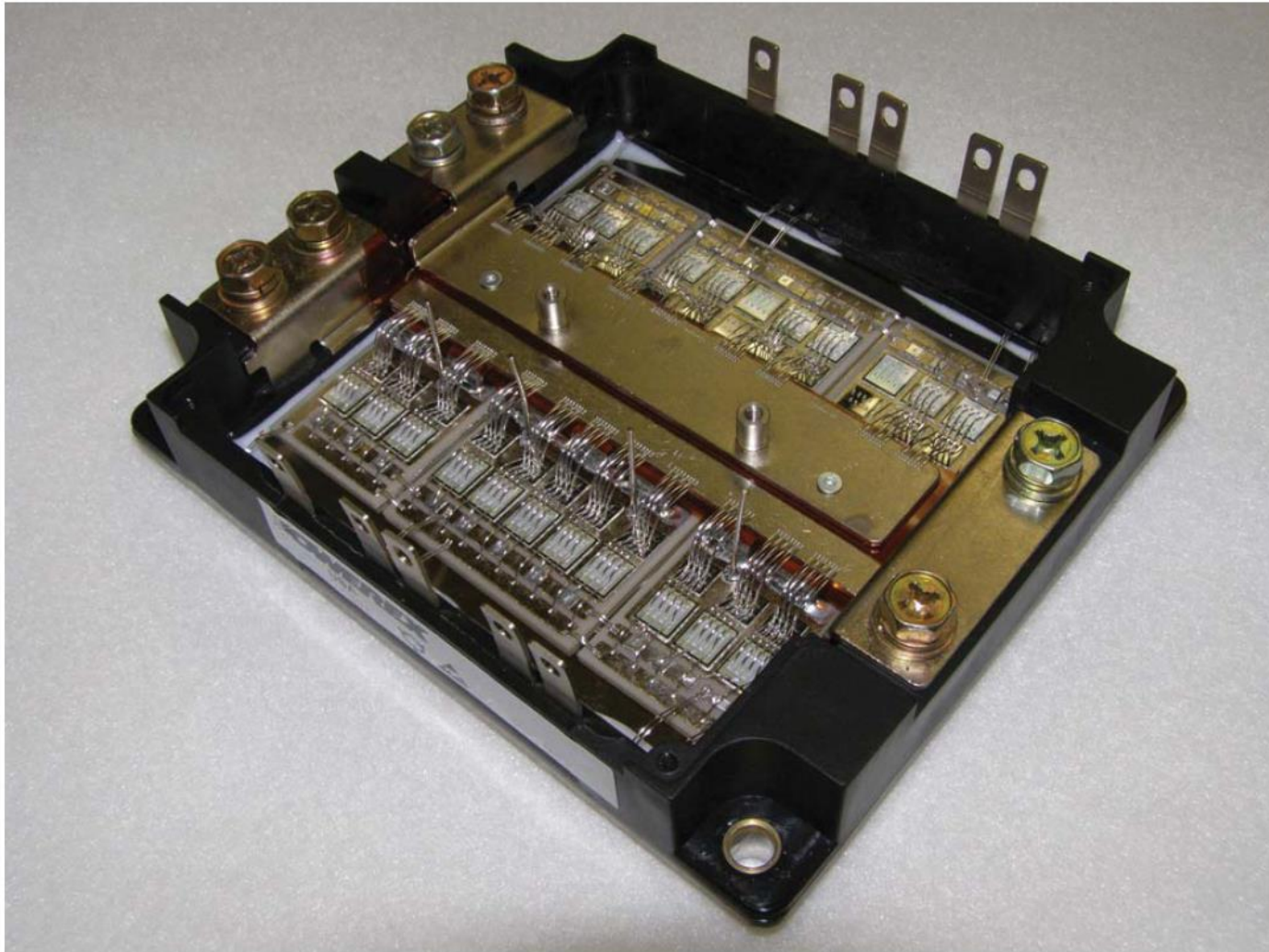
# 1.2-kV, 800-A SiC-MOSFET/SBD Dual Module



R. Wood and T. Saken, "Evaluation of a 1200-V, 800-A All-SiC Dual Module,"


35

IEEE Trans. on Power Electronics, vol. 26, no. 9, 2011

*Tokyo Institute of Technology*  
*Power Electronics Lab.*



# Bidirectional Isolated DC-DC Converter

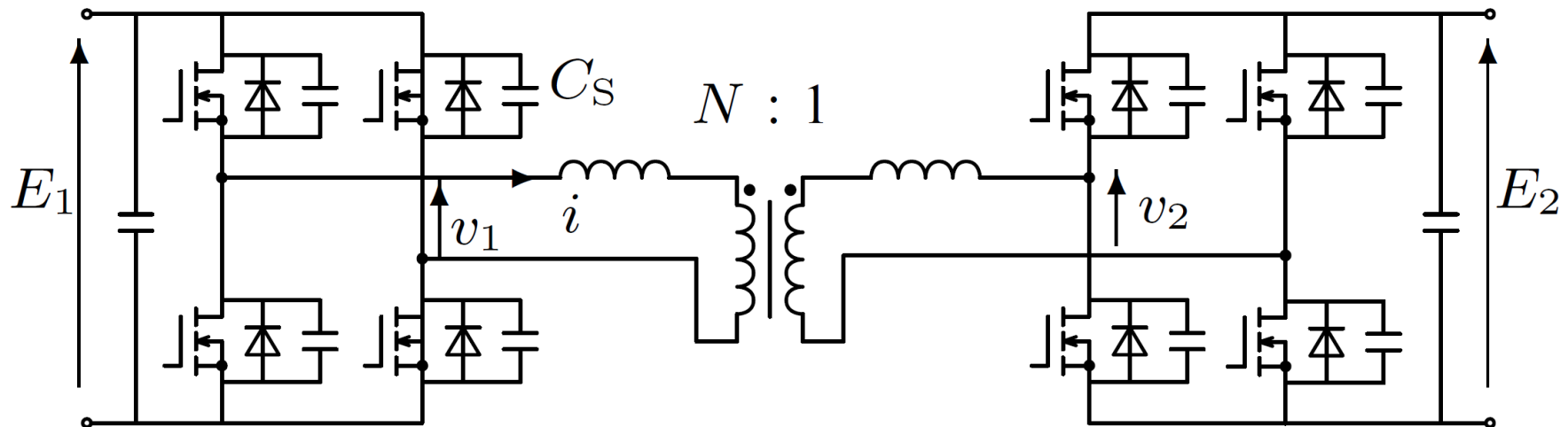

## Two Technical Terms

**Functionality:** Bidirectional Isolated DC-DC Converter

**Circuit Topology:** Dual-Active-Bridge Converter

## Function/Operation

**Both buck and boost function:**  $E_1 > E_2$  and  $E_1 < E_2$  When  $N=1$

**Zero-voltage-switching (ZVS) operation**

**Synchronous Rectification (limited to Si and SiC MOSFETs)**

R. W. De Doncker, D. M. Divan, and M. H. Khealuwala, *IEEE Trans. IA*, 1991.


Tokyo Institute of Technology  
Power Electronics Lab.



# Experimental System at 750 V, 100 kW, and 20 kHz

1.2-kV, 400-A SiC-MOSFET/SBD Module

$P$   
←

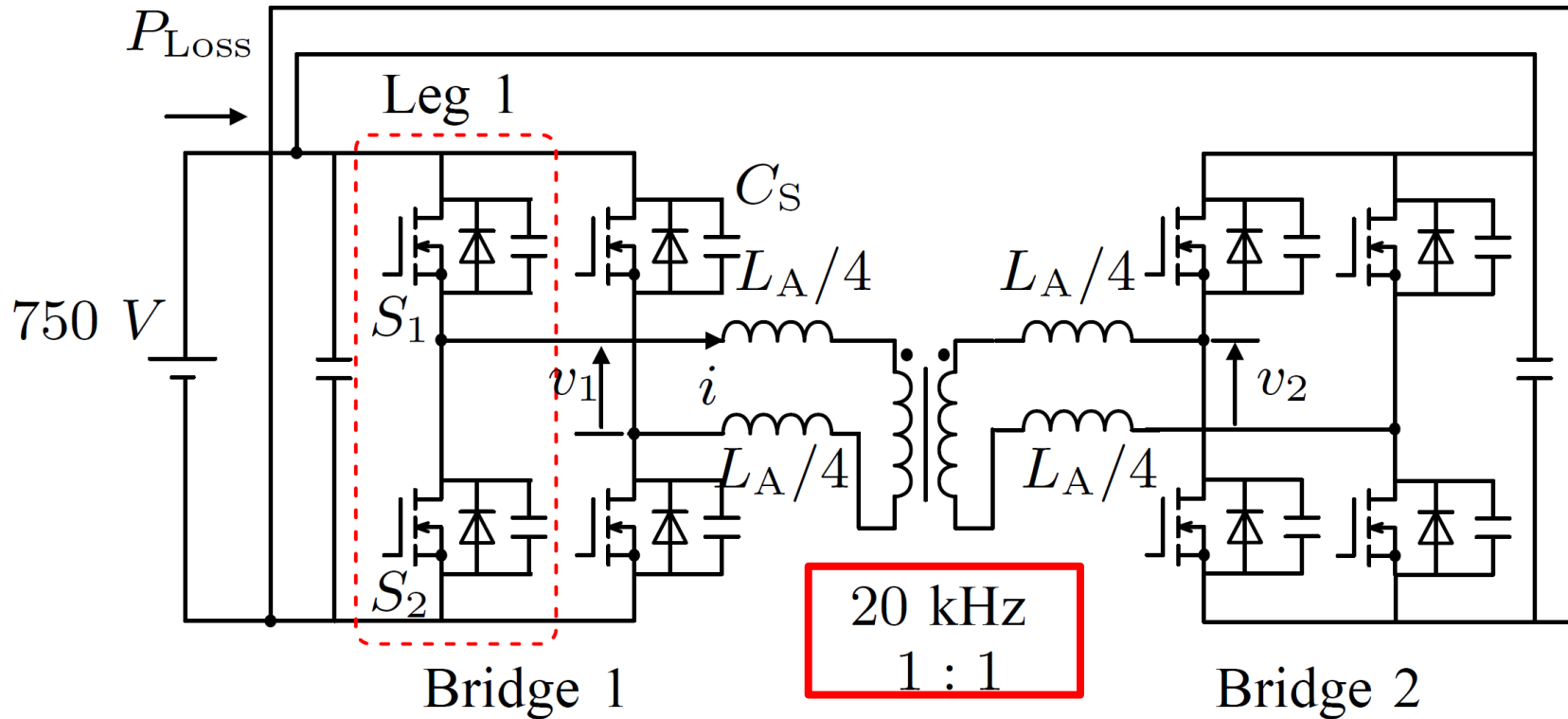


Converter (dc-to-dc) efficiency  
with a tolerance of 0.03%

$$\eta = \frac{P}{P + P_{Loss}}$$



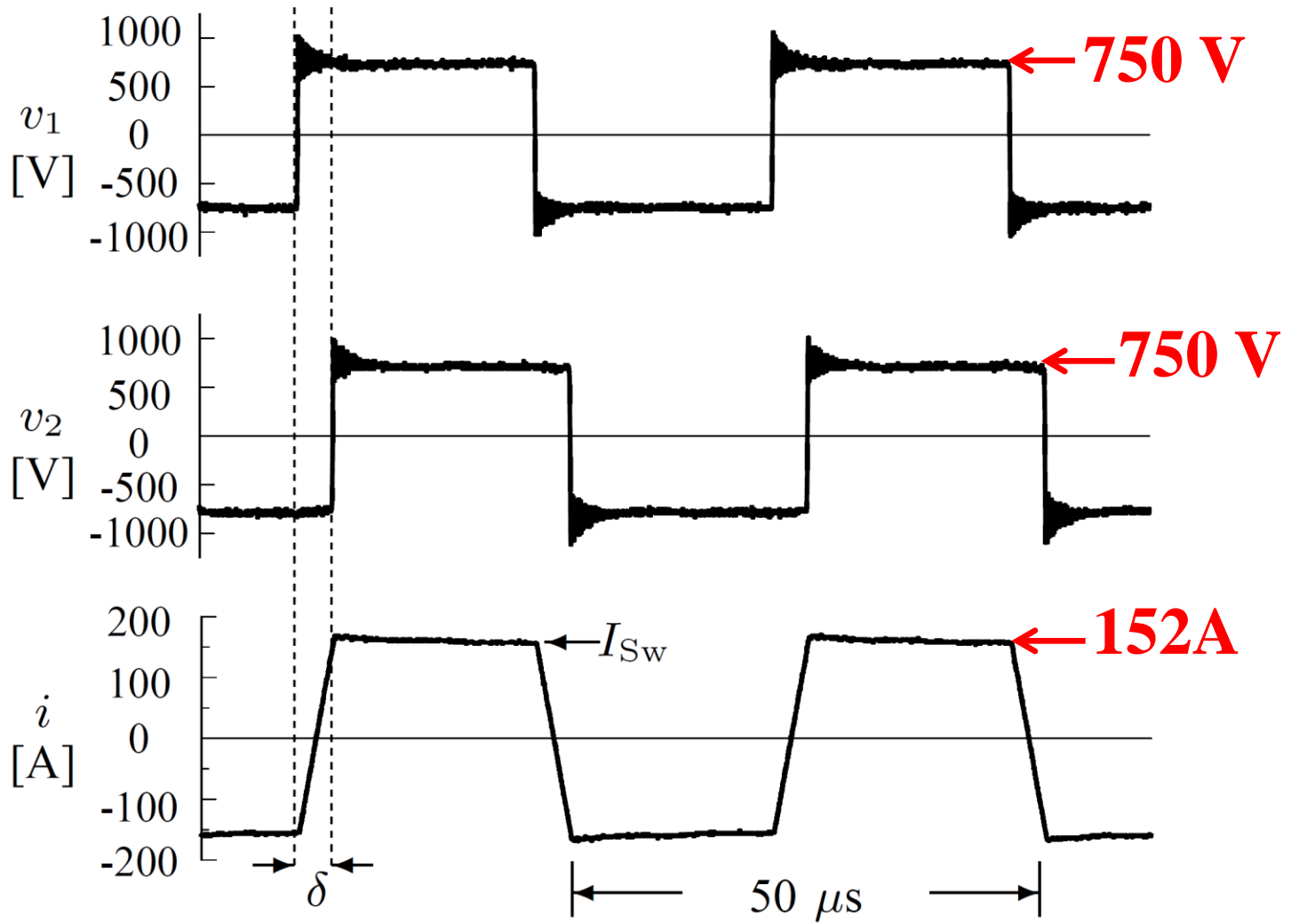
# Experimental Waveforms at 750 Vdc and 100 kW



$$T_D = 0.6 \mu s \quad \delta = 26.6^\circ$$




# Power Loss and Efficiency

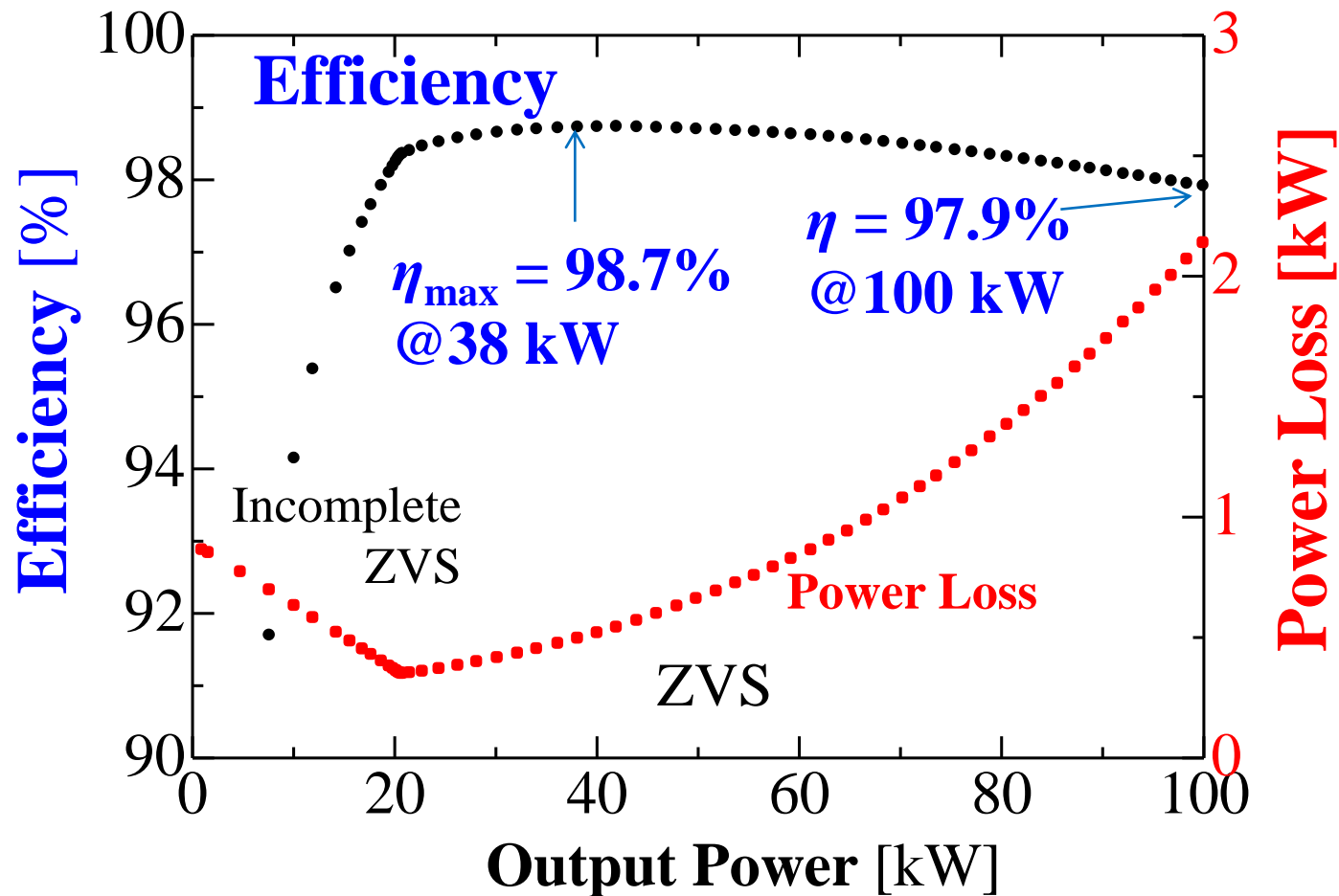

- Maximum Efficiency: **98.7 %**
- Rated-Power Efficiency: **97.9%**


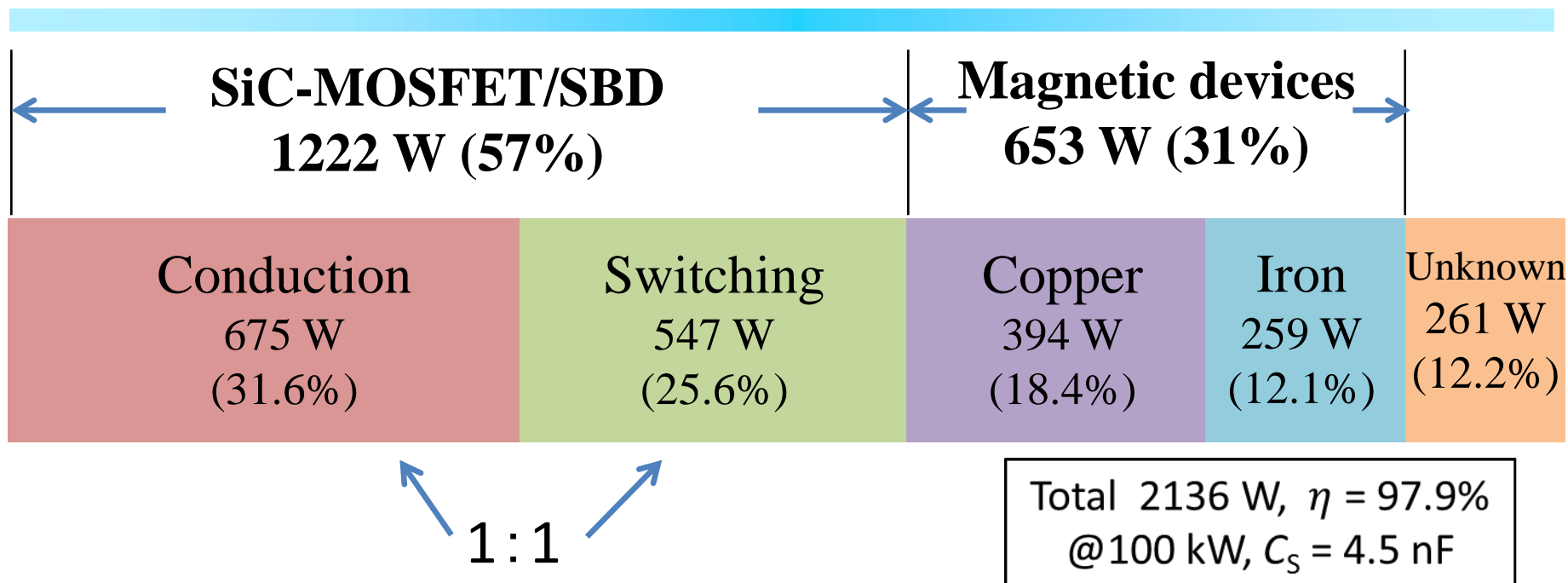
# Power-Loss Breakdown at 100-kW Operation



- Power Loss in SiC-MOSFET/SBD: 60%
- Power Loss in Magnetic Devices: 30%
- Conducting and Switching Losses are Nearly Equal.





# SiC-MOSFET/SBD and Si-IGBT/PND Modules


	SiC- MOSFET/SBD Dual Modules	Si-IGBT/PND Dual Modules <sup>(1)</sup>
Power rating	<b>100 kW</b>	60 kW
Reference voltage	750 Vdc	750 Vdc
Frequency	<b>20 kHz</b>	4 kHz
Power device	1.2 kV and <b>400 A</b>	1.2 kV and 300 A
Maximum efficiency	<b>98.7%</b>	97.8%
Rated-Power Efficiency	<b>97.9%</b>	96.9%

(1) T. Chocktaweechock, K. Hasegawa, and H. Akagi, *IEEJ IAS Annual Meeting*, 1-94, Aug. 2012

**Both dual modules have the same packaging in size, shape and pin/terminal arrangement.**


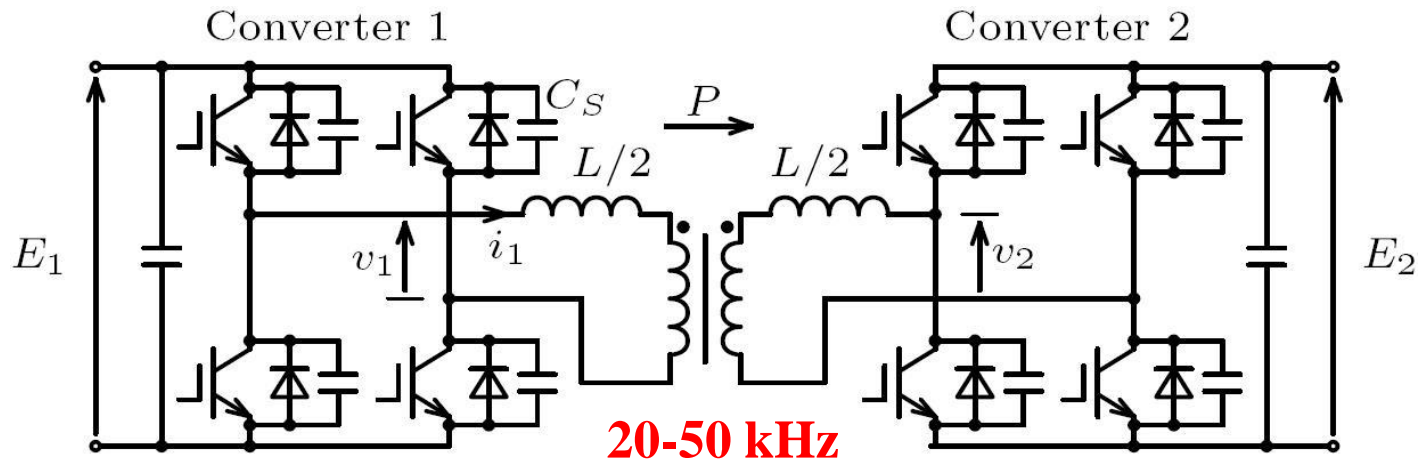
# Past, Present, and Future of the DC-DC Converters



(1) M. H. Kheraluwala, et al., *IEEE Trans. Ind. Applicat.*, vol. 28, no. 6, pp. 1295-1301, **1992**

	1990 <sup>(1)</sup>	2014 (Tokyo Tech)	<b>2020?</b>
<b>Switching Devices</b>	Planar-Gate IGBTs	Planar-Gate SiC-MOSFETs	<b>Trench-Gate SiC-MOSFETs</b>
<b>Core Material in Transformer</b>	Ferrite	FINEMET™*	<b>New Magnetic Materials</b>
<b>Efficiency (DC to DC)</b>	Below 90% @50 kW, 50 kHz	98% @100 kW, 20 kHz	<b>Over 99%</b> <b>@100 kW, 20 kHz</b>

\* Nano-crystalline soft-magnetic material from Hitachi Metals



# What I want to emphasize

---

Power electronics people have been making a long voyage

from a **Silicon planet** to a **Silicon-Carbide planet**.

It will take five years from now to complete the wonderful voyage. This completion, as well as

**the continuous development of “Control”**

**by leaps and bounds,**

will bring a new world to power electronics.

